

C&S LE Sessional exam

Total points 27/30 ?

Email address *

atulmahto201@gmail.com

Name *

ATUL MAHTO KHARIA

Class *

EEE ▼

✓ A time invariant system is a system whose output *

3/3

- ☐ increases with a delay in input
- ☐ decreases with a delay in input
- ☒ remains same with a delay in input
- ☐ vanishes with a delay in input



✓ A system is said to be defined as non causal, when *

3/3

- ☐ the output at the present depends on the input at an earlier time
- ☐ the output at the present does not depend on the factor of time at all
- ☐ the output at the present depends on the input at the current time
- ☒ the output at the present depends on the input at a time instant in the future



✓ Which among the following is a LTI system? *


3/3

- ☐ $dy(t)/dt + ty(t) = x(t)$
- ☐ $y(t) = x(t) \cos \pi t$
- ☐ $y(n) = x(n) + nx(n-1)$
- ☒ $y(n) = x^3(n+1)$



✓ For the circuit given below, the Time-constant is _____ *

3/3

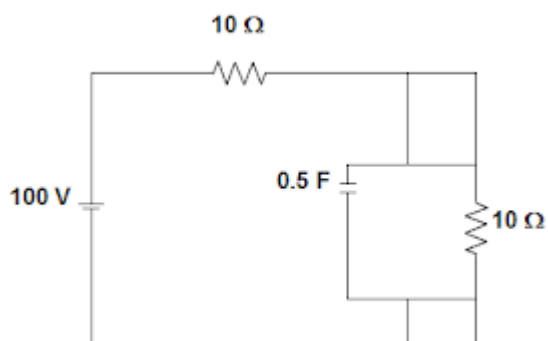


- ☐ 1.5
- ☒ 1.25
- ☐ 2.5
- ☐ 2.25



✗ Express the waveform shown by the standard signals *

0/3

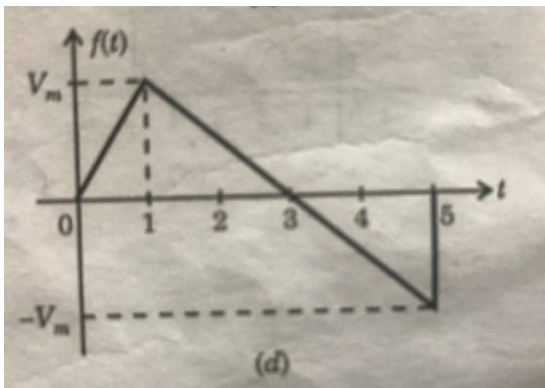

- ☐ $V_m r(t) - \frac{3}{2} V_m r(t-1) + \frac{V_m}{2} r(t-5) + V_m U(t-5)$
☐ $V_m r(t) - \frac{3}{2} V_m r(t-1) + \frac{V_m}{2} r(t-5)$
☐ $V_m r(t) + V_m U(t-5)$
☒ $V_m r(t) - \frac{3}{2} V_m r(t-1) + \frac{V_m}{2} r(t-5) + V_m U(t-5) + V_m r(t+5)$

✗

Correct answer

- ☒ $V_m r(t) - \frac{3}{2} V_m r(t-1) + \frac{V_m}{2} r(t-5) + V_m U(t-5)$

✓ Find the initial value of the signal given below $F(t) = [e^{-2t} + e^{-t} \cos 3t] U(t)$ *


3/3

- ☐ 0
☐ 1
☒ 2
☐ ∞

✓



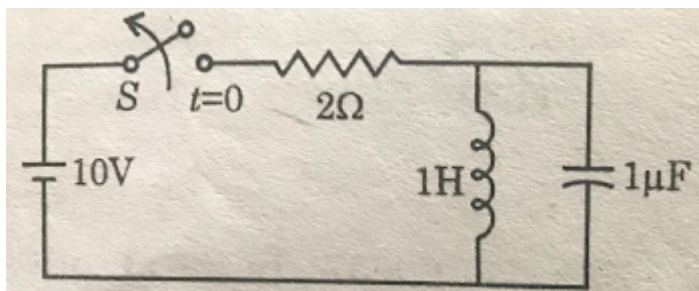- ✓ In the circuit, switch S is closed and steady state conditions reached. 3/3
 Now at time $t=0$, switch S is opened. What is the expression for the current through the inductor? *



- ☐ $I(t) = 5\text{A}$
- ☐ $I(t) = 6.5\text{A}$
- ☒ $i(t) = 5 \cos 1000t\text{A}$
- ☐ ∞



- ✓ The step voltage applied to a series R-L circuit is 36V with $R = 15\text{ Ohms}$. 3/3
 Determine the value of inductance L required to make the current of 1.0A at 250 μsecs . Assume the initial current is zero. *

- ☐ 4.56 H
- ☒ 6.957 H
- ☐ 7.2 H
- ☐ 2.1 H



✓ At $t = 0^+$, with zero initial condition which of the following will act as short circuit *

☐ Inductor

☒ Capacitor

☐ Resistor

☐ None of these



✓ At very low frequencies a series R-C circuit behaves as almost purely *

3/3

☐ Resistive

☐ Inductive

☒ Capacitive

☐ None of these



This form was created inside of Maharaja Surajmal Institute of Technology.

Google Forms

